

7447 through AVR-Assembly

G V V Sharma*

CONTENTS

1	Components	1
2	Controlling the Display	1
<i>Abstract</i> —This manual shows how to program the 7447 BCD-Seven segment display decoder through AVR-Assembly.		

1 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

2 CONTROLLING THE DISPLAY

1. Connect the 7447 IC to the seven segment display.
2. Make connections between the 7447 and the arduino according to Table ??

7447	D	C	B	A
Arduino	5	4	3	2

TABLE 2

3. Now generate the numbers 0-9 by modifying the above program.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.