

# Decade Counter through 7474 and AVR-Assembly

G V V Sharma\*

## CONTENTS

1	Components	1
2	Decade Counter	1
	References	1
	<i>Abstract</i> —This manual shows how to build a decade counter using the 7474 D-Flip Flops through AVR-Assembly.	

## 1 COMPONENTS

Component	Value	Quantity
Breadboard		1
Resistor	$\geq 220\Omega$	1
Arduino	Uno	1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
Jumper Wires		20

TABLE 0

## 2 DECADE COUNTER

- 1) Connect the Arduino, 7447 and the two 7474 ICs according to Table 1 and Fig. 1.
- 2) Intelligently use the codes in [1], [2] to realize the decade counter in Fig. 1.

## REFERENCES

- [1] G. V. V. Sharma. 7447 through AVR-Assembly. [Online]. Available: [https://github.com/gadepall/arduino/raw/master/assembly/7447/io/gvv\\_ard\\_assembly\\_7447.pdf](https://github.com/gadepall/arduino/raw/master/assembly/7447/io/gvv_ard_assembly_7447.pdf)
- [2] ——. Boolean Logic through AVR-Assembly. [Online]. Available: [https://github.com/gadepall/arduino/raw/master/assembly/7447/count/gvv\\_ard\\_assembly\\_7447\\_count.pdf](https://github.com/gadepall/arduino/raw/master/assembly/7447/count/gvv_ard_assembly_7447_count.pdf)

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

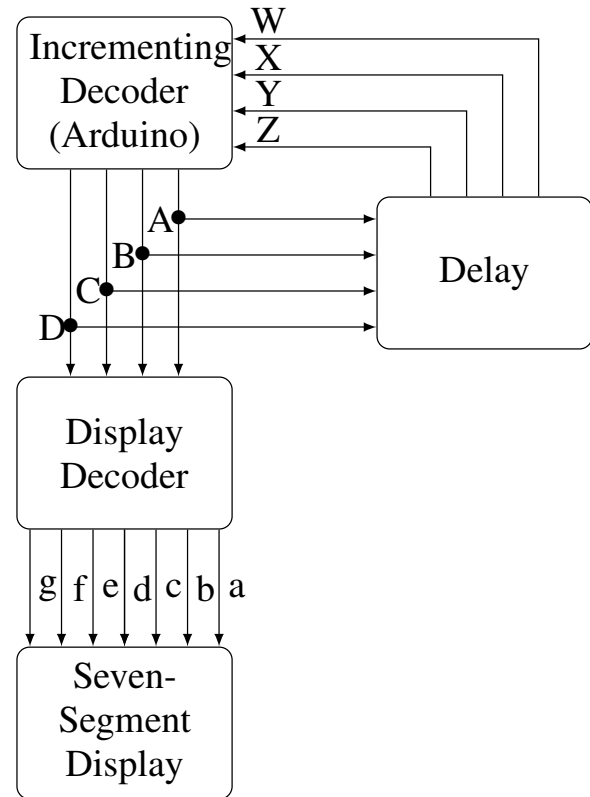


Fig. 1

	INPUT				OUTPUT				CLOCK	5V				
	W	X	Y	Z	A	B	C	D						
Arduino	8	9	10	11	2	3	4	5	13					
7474	5	9			2	12			CLK1	CLK2	1	4	10	13
7474			5	9			2	12	CLK1	CLK2	1	4	10	13
7447					7	1	2	6			16			

TABLE 1